

Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I
Date of Performance:	30/ 10/ 2023	Batch No:	C5_1
Faculty Name:	Mr. Sandeep Hanumante	Roll No:	16010123293
Faculty Sign & Date:		Grade/Marks:	/ 25

Experiment No: 7

Title: Measurement of Power using Two Wattmeter Method


Aim and Objective of the Experiment:

- To measure the power of three phase power using Two Wattmeter Method

COs to be achieved:

CO2: Demonstrate and analyze steady state response of single phase and three phase circuits

Circuit Diagram:

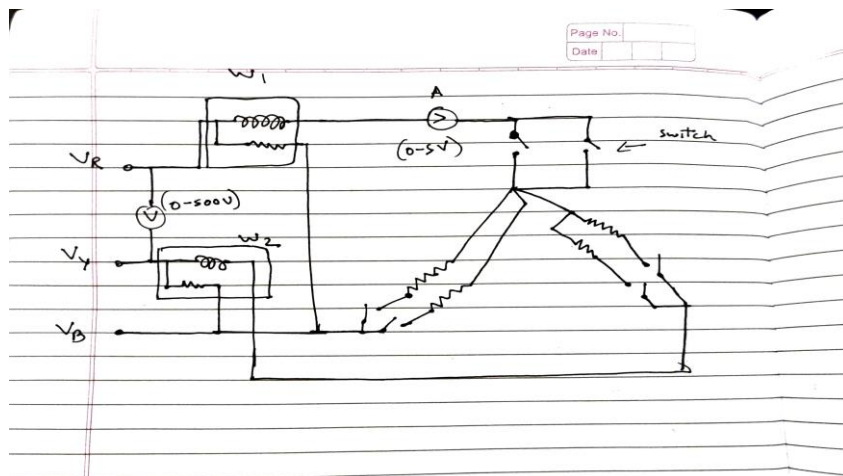

Stepwise-Procedure:

1. Connect the circuit as shown in circuit diagram
2. Increase the load and note down the reading V_L, I_L, W_1 and W_2
3. Practically you will obtain total power $W = W_1 + W_2$
4. Theoretically power is measured by using formula $P = \sqrt{3} V_L I_L \cos \phi$,
using $\cos \phi = 1$ (unity) for resistive load.

Observation Table:

Sr.no	V_L (Volts)	I_L (Amp)		W_1 (KW)		W_2 (KW)		$P_T = (W_1 + W_2)$ (KW)	
		TH	PR						
1	405	0.88	0.80	240		360		600	
2	405	1.75	1.28	480		680		1160	

Theoretical Calculations:

$$\text{Power} = \sqrt{3} \times V_L \times I_L \times \cos \phi$$

$$\cos \phi = 1$$

$$\text{Power} = \text{Wattage rating of lamp load} \times \text{No of lamps (One lamp is of 100W rating)}$$

$$W_1 = V_L \times I_L \times \cos (30 + \phi)$$

$$\Phi = 0$$

$$W_2 = V_L \times I_L \times \cos (30 - \phi)$$

$$\text{Total Power} = P = W_1 + W_2$$



Conclusion:

Measured the power of three phase power using two wattmeter method. Practically analyzed steady state response of single phase and three phase circuits.

Signature of faculty in-charge with Date: